



WEST BENGAL STATE UNIVERSITY
B.Sc. Honours 4th Semester Examination, 2020

ELSACOR10T- ELECTRONICS (CC10)

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.*

Answer Question No. 1 and any two from the rest

GROUP-A

1. Answer any *five* questions from the following: 2×5 = 10
- (a) State one difference between active and passive probe.
 - (b) What is the function of aquadag in CRO?
 - (c) State two advantages of R-2R ladder over weighted-resistor method.
 - (d) Define an active transducer.
 - (e) Define (i) Resolution and (ii) Accuracy of a measuring instrument.
 - (f) What is the function of a blanking circuit in a CRO?
 - (g) What is the drawback of rectifier-type a.c. voltmeter?
 - (h) State one reason why Hay's bridge is preferred over Maxwell's Bridge.

GROUP-B

2. (a) With a neat sketch, explain construction and working of an LVDT. 8
- (b) What is gauge factor? Derive an expression of gauge factor and prove that $k = 1 + 2\mu$. 7
3. (a) Derive with necessary diagram expression for self-inductance and resistance of an unknown inductor using Anderson's bridge. 8
- (b) Draw diagram of a 4-bit weighted resistor Digital to Analog converter and derive Expression for its resolution. 7

4. (a) Explain electrostatic focusing system in a C.R.O. 6
- (b) Draw the block diagram of the Horizontal deflection system in a C.R.O. What is the need for a delay line? 2+2
- (c) Explain working of time-base generator circuit. 5
5. (a) A basic D'Arsonval movement with an internal resistance of 50Ω and a full-scale deflection current of 2mA is to be converted to a voltmeter with a range $0-10\text{V}$. Determine the resistance required. 4
- (b) Explain working of a true-RMS voltmeter with necessary diagram. 6
- (c) Draw the block diagram and explain the working principle of successive approximation type DVM. 5

N.B. : *Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.*

—X—