



WEST BENGAL STATE UNIVERSITY
B.Sc. Honours/Programme 4th Semester Examination, 2020

CMSGEC04T/CMSGCOR04T-COMPUTER SCIENCE (GE4/DSC4)

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.
All symbols are of usual significance.*

Answer Question No. 1 and any four questions from the rest

GROUP-A

1. Answer any **four** questions from the following: 2×4 =8
- (a) What are the differences between time-sharing system and multiprogramming system?
- (b) Simplify the given expression using Boolean Algebra
$$A + AB' + A'B$$
- (c) How does the floating-point number represents in computer system?
- (d) What is the function of DMA?
- (e) What is Peripheral Component Interconnect (PCI)?
- (f) Write down the generic expression to convert (number)_x to (number)_y, where x and y are bases.
- (g) Why MUX is functionally complete?
- (h) What is a modulus counter?

GROUP-B

Answer any four questions from the following

8×4 = 32

2. (a) Define a decoder. 2
- (b) Draw the logic diagram of a 3-to-8 decoder. 3
- (c) What is the advantage of 2's complement system over 1's complement? Using 2's complement add $(+38)_{10}$ and $(-22)_{10}$. 3

3. (a) The ALU of an IAS computer contains a Memory Buffer Register (MBR) , an Accumulator (AC) and a Multiplier-Quotient (MQ) and the Program Control Unit (CU) contains a Memory Address Register (MAR), an Instruction Register (IR), and a Program Counter (PC). Explain the functionality of each unit. 6
- (b) Write down the behavior of a tri-state switching device. 2
4. (a) Discuss about different modes of data transfer inside a simple computer system. 5
- (b) What is SCSI? How does SCSI differs from PCI? 3
5. (a) Define flip-flop. 2
- (b) What is SR flip-flop? Draw NAND-based SR flip-flop. 2+2
- (c) Write down the basic applications of flip-flop. 2
6. (a) Design a counter which counts 0, 1, 2, 3, 4, 5, 6, 7 sequentially. 4
- (b) Simplify the following Boolean expression: $f(a, b, c, d) = \Sigma(0,1,2,3,7,11,15)$ in SOP form. 4
7. (a) Explain One and Zero address instructions with suitable example. 4
- (b) Describe Register Indirect and Immediate addressing modes with proper example. 4
8. (a) Simplify the expression $Y = \Sigma m(7, 9,10,11,12,13,14,15)$ using the K-map method. 4
- (b) Discuss any two Memory-reference instructions. 4

N.B. : *Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.*

—×—