



WEST BENGAL STATE UNIVERSITY
B.Sc. Honours 3rd Semester Examination, 2020, held in 2021

ELSACOR05T-ELECTRONICS (CC5)

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.
All symbols are of usual significance.*

SECTION-A

1. Answer any **five** questions from the following: 2×5 = 10
- (a) In a half wave rectifier circuit, the V_{\max} of the applied input ac voltage is 12 V. Find the V_{DC} and V_{RMS} .
 - (b) Why the emitter region of a transistor is more heavily doped than the base region?
 - (c) When operated as a switch, which regions does a BJT switches between?
 - (d) What is the necessity of using a filter in a rectifier?
 - (e) What do you mean by Peak Inverse Voltage of a P-N junction diode?
 - (f) A 4.7 V 0.25 Watt Zener diode is used as a voltage regulator. Calculate the value of resistor required in series with the Zener diode, if the maximum input voltage is 6 V.
 - (g) Draw the circuit diagram of a bridge rectifier circuit.
 - (h) Define the current amplification factor α and β of a transistor and write the relation between them.

SECTION-B

Answer any six questions from the following

5×6 = 30

2. (a) Draw the different current components in a $n-p-n$ transistor, biased in active mode of operation. 2
- (b) Derive the relationship $I_c = \beta I_b + (1 + \beta) I_{CO}$, where the symbols have their usual meanings. 3
3. What is ripple factor? How can it be removed or minimized using a Π type filter? 2+3
4. (a) Make a comparative study of Q -point stability in the fixed bias and self-bias circuit. 3
- (b) Draw the equivalent circuit diagram of a small-signal low frequency CE transistor amplifier. 2

5. Draw the circuit and explain the operation of a shunt capacitor filter with waveforms. 5
6. A silicon $n-p-n$ transistor with $\alpha = 0.995$ and $I_{co} = 15$ nA, operates in the CE configuration. What is the collector current for a base current of $20 \mu\text{A}$? 5
7. What do you mean by Base width Modulation and punch through effect in bipolar junction transistor? 5
8. Write a short note on Darlington Pair. 5
9. Deduce the Hybrid Parameters for a BJT in CE Mode from the concept of Two-Port Network. 5
10. What are the load and line regulation characteristics of a Zener diode? Write two disadvantages of Zener diode regulator. 3+2

N.B. : *Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.*

—×—