



**WEST BENGAL STATE UNIVERSITY**  
B.Sc. Honours 3rd Semester Examination, 2021-22

**ELSACOR06T-ELECTRONICS (CC6)**

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.  
Candidates should answer in their own words and adhere to the word limit as practicable.  
All symbols are of usual significance.*

**GROUP-A**

1. Answer any **five** questions from the following: 2×5 = 10
- (a) How can an EX-OR gate be used as a controlled inverter?
  - (b) Realise a three input NAND gate using two input NAND gates only.
  - (c) Define fan-out of a gate.
  - (d) How can a decoder be used as a de-multiplexer?
  - (e) Convert a J-K flip-flop to a D flip-flop.
  - (f) Convert the binary number 101100110 to Gray-code.
  - (g) Express two numbers 926 and 827 in BCD form and add them.
  - (h) Do the following subtraction using 2's complement 72–48.

**GROUP-B**

**Answer any six questions from the following**

**5×6 = 30**

2. (a) If  $Y = A'B + BC$ , express  $Y$  in POS form. 3+2  
(b) Subtract 10110 – 11011 using 2's complement method.
3. (a) Show that a negative logic OR gate is equivalent to a positive logic AND gate. 2+3  
(b) Design a EX-OR gate using NAND gates only.
4. (a) Realise a 2-input 1+2+2  
(i) OR gate  
(ii) NAND gate using 2:1 MUX only  
(b) Realise the function  $Y = \sum m(1, 2, 4, 7, 9, 13, 15)$  using a 8:1 MUX

5. (a) Explain 'Race' condition in a S-R flip-flop. 2+3  
(b) Design a J-K flip-flop using an S-R flip-flop.
6. Design a 3 to 8 line active low decoder using NAND gates only. 5
7. Explain the following:  $2\frac{1}{2} + 2\frac{1}{2}$   
(i) Entity Declaration  
(ii) Architecture Declaration.
8. (a) Explain the difference between an encoder and a priority encoder. 2+3  
(b) Design a 2-bit priority encoder.
9. Explain the Data Flow modeling scheme using suitable example. 5

**N.B. :** *Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.*

—×—