



WEST BENGAL STATE UNIVERSITY
B.Sc. Honours 1st Semester Examination, 2021-22

ELSACOR01T-ELECTRONICS (CC1)

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.
All symbols are of usual significance.*

GROUP-A


1. Answer any *five* questions from the following: 2×5 = 10
- What is the 'time constant' of a RC circuit?
 - Show that the voltage across an inductor leads the current by a phase angle of 90° .
 - A circular ring is made of a continuous wire of resistance 12Ω . The equivalent resistance between two points P and Q on the ring is $\frac{8}{3} \Omega$. Find the ratio of wire lengths (longest to shortest) between the points P and Q .
 - "In a DC circuit, an inductor behaves as a resistor" — Explain the statement.
 - State Millman's theorem.
 - Why do we express AC voltages/currents in terms of rms values?
 - "Thevenin's Theorem cannot be applied to a circuit which contains a diode" — Explain.
 - Define: (i) Symmetric and (ii) Reciprocal network.
 - A 25Ω resistance has a voltage $v = 150\sin(377t)$ V. Find the average power delivered by the voltage sources in one complete cycle.

GROUP-B


Answer any *six* questions from the following

5×6 = 30

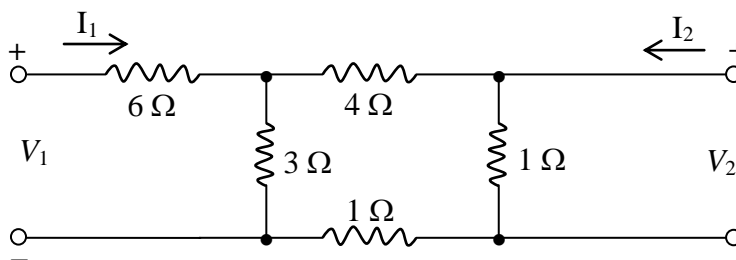
2. Find the Z parameters of the network shown below. 5



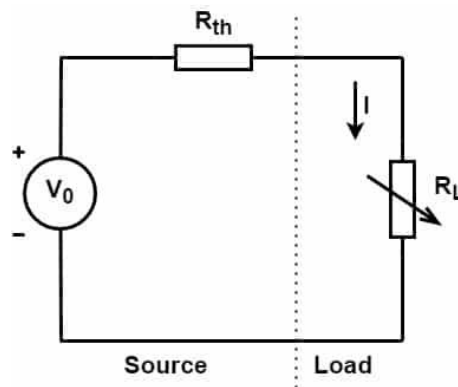3. (a) Find relationship between bandwidth and quality factor. 3
 (b) Show that the resonant frequency is the geometric mean of the half power frequency. 2
4. (a) Derive the transient response (growth OR decay) of a DC series L-R circuit. 3
 (b) For parallel combination of two inductors L_1 and L_2 , show that the effective inductance (L) is given by $\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$ (ignore the mutual inductance between L_1 and L_2). 2
5. (a) A typical circuit is shown below. Show that the maximum power is transferred when $R_L = R_{Th}$. Further, show that the maximum power transferred to load resistance R_L is $\frac{V_{Th}^2}{4R_{Th}}$. 3




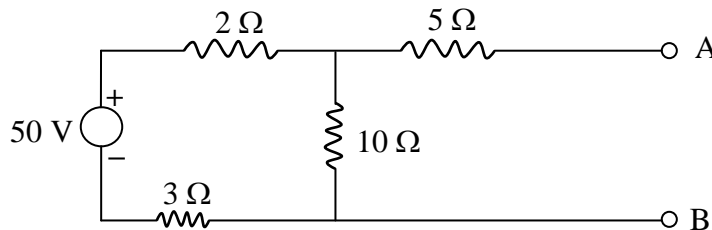- (b) For the following circuit, find the value of resistance to be connected at A – B so that maximum power is transferred by the source. What is maximum power? 1+1




6. (a) Find the expression for resonant frequency of a parallel RLC circuit. 3
 (b) Compare in brief, the series and parallel resonance. 2
7. (a) What is meant by a Ideal Current Source? 2
 (b) How a ideal current source differ from a ideal voltage source? 2
 (c) What is a dependent energy source? 1
8. (a) Find expression for output voltage of a low pass filter. 2
 (b) Show how it works on 2+1
 (i) Phase-Log circuit
 (ii) Integrator.

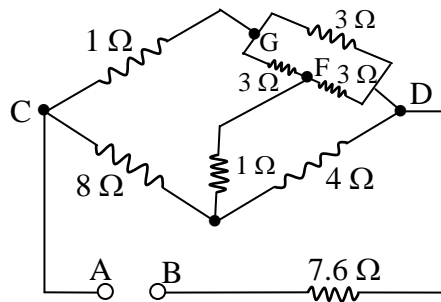9. Find the equivalent resistance across the terminals A and B (you may use star-delta or delta-star conversion). 5



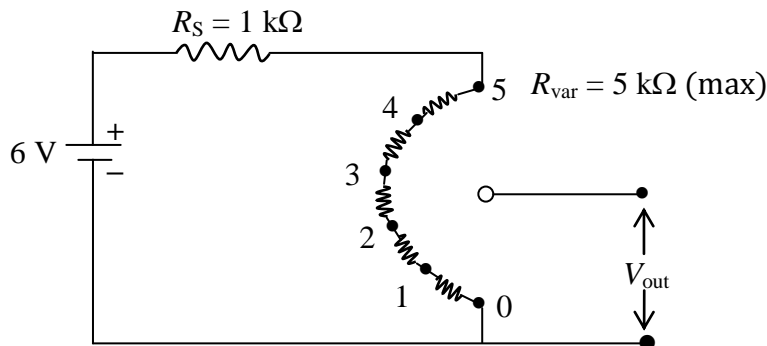10. A DC circuit is shown below. In this circuit, the variable resistance R_{var} is equally divided among the positions labelled by 0 to 5.
- (a) Find the position of the R_{var} for maximum V_{out} . 1
- (b) Find the current flowing through the circuit for the case stated above. 1
- (c) Let the position of the variable resistor be at 2, and consider a load resistance of 2Ω (not shown in the figure) is connected across V_{out} . Under such condition, find 3
- (i) V_{out} ,
- (ii) current through R_S and
- (iii) current through the load resistance.



- 11.(a) Why impedance is complex? 1
- (b) What are the real and imaginary parts of a complex impedance called? 2
- (c) Define power factor. 2

N.B. : Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.

—x—