



## WEST BENGAL STATE UNIVERSITY

B.Sc. Honours 4th Semester Examination, 2022

### ELSACOR08T-ELECTRONICS (CC8)

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.  
Candidates should answer in their own words and adhere to the word limit as practicable.  
All symbols are of usual significance.*


#### GROUP-A

1. Answer any **five** questions from the following: 2×5 = 10
  - (a) What is the cause of slow rate in an OP-AMP? 2
  - (b) How does CMRR of OP-AMP vary with frequency? 2
  - (c) What is the utility of an unity-gain buffer? 2
  - (d) Why are dual power supply voltages provided to an OP-AMP? 2
  - (e) Find input impedance of inverting amplifier using OP-AMP. 2
  - (f) Why is a stable multivibrator called as free running multivibrator? 2
  - (g) Write down the significance of zero output impedance of an ideal OP-AMP. 2
  - (h) State any two factors responsible for offset voltage in an OP-AMP. 2

#### GROUP-B


**Answer any six questions from the following** 5×6 = 30

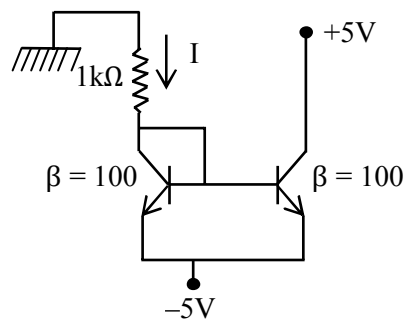2. Derive the condition of oscillation in a Wien-bridge oscillator. Hence explain how amplitude stabilization is achieved in an OP-AMP based implementation of the oscillator. 3+2
3. Realise a bistable multivibrator using IC 555 and explain its operation. 2+3
4. (a) Show that the circuit functions as a current mirror and find the value of I. 4




- (b) Define PSRR of an OP-AMP. 1
5. (a) Find expression for the gain of a non-inverting amplifier assuming the gain to be finite. 3

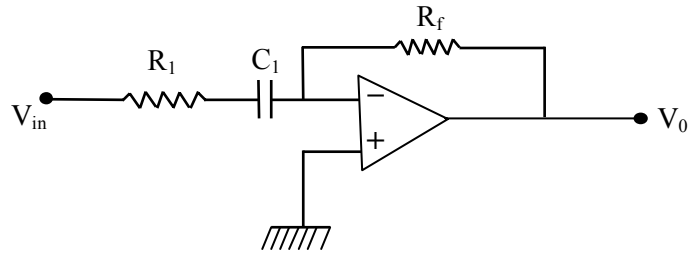- (b) Explain with reason, the type of filter realized by the given circuit. 2



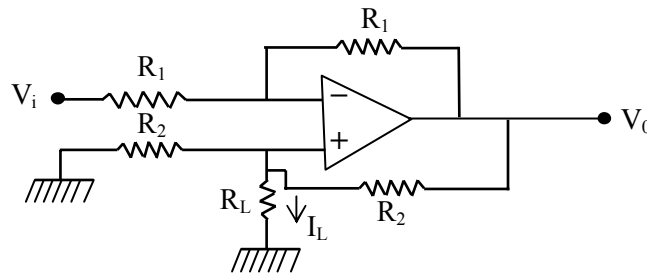6. (a) Find the value of  $I_L$  in the given circuit. 3



- (b) What are the unique characteristics of differential amplifier? 2
7. Describe how an OP-AMP can be used as a square-wave generator and find out the expression of frequency of the output. 5
8. (a) Explain with a block diagram, how OP-AMPs can be used for multiplication of two voltages. 3  
 (b) Draw and explain the transfer characteristics of an OP-AMP. 2
9. (a) Find expression for output voltage of a practical integrator. 3  
 (b) What are the advantages of active filter over passive filter? 2
- 10.(a) For a similar gain, explain the advantage of non-inverting mode over non-inverting mode of operation. 2  
 (b) Draw a labelled block diagram of the different stages of an OP-AMP and explain the function of each stage. 3
- 11.(a) Design a practical integrator that integrates signals with frequency down to 500 Hz. It produces a peak output of 0.5 V when the input is a sine wave with a peak amplitude of 10 V with a frequency of 10 kHz. 3  
 (b) Design an active first order low pass butterworth filter with cut-off frequency 1 kHz and for a given gain 3.2 (Given  $C = 0.1 \mu\text{F}$ ). 2

**N.B. :** Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.

—x—